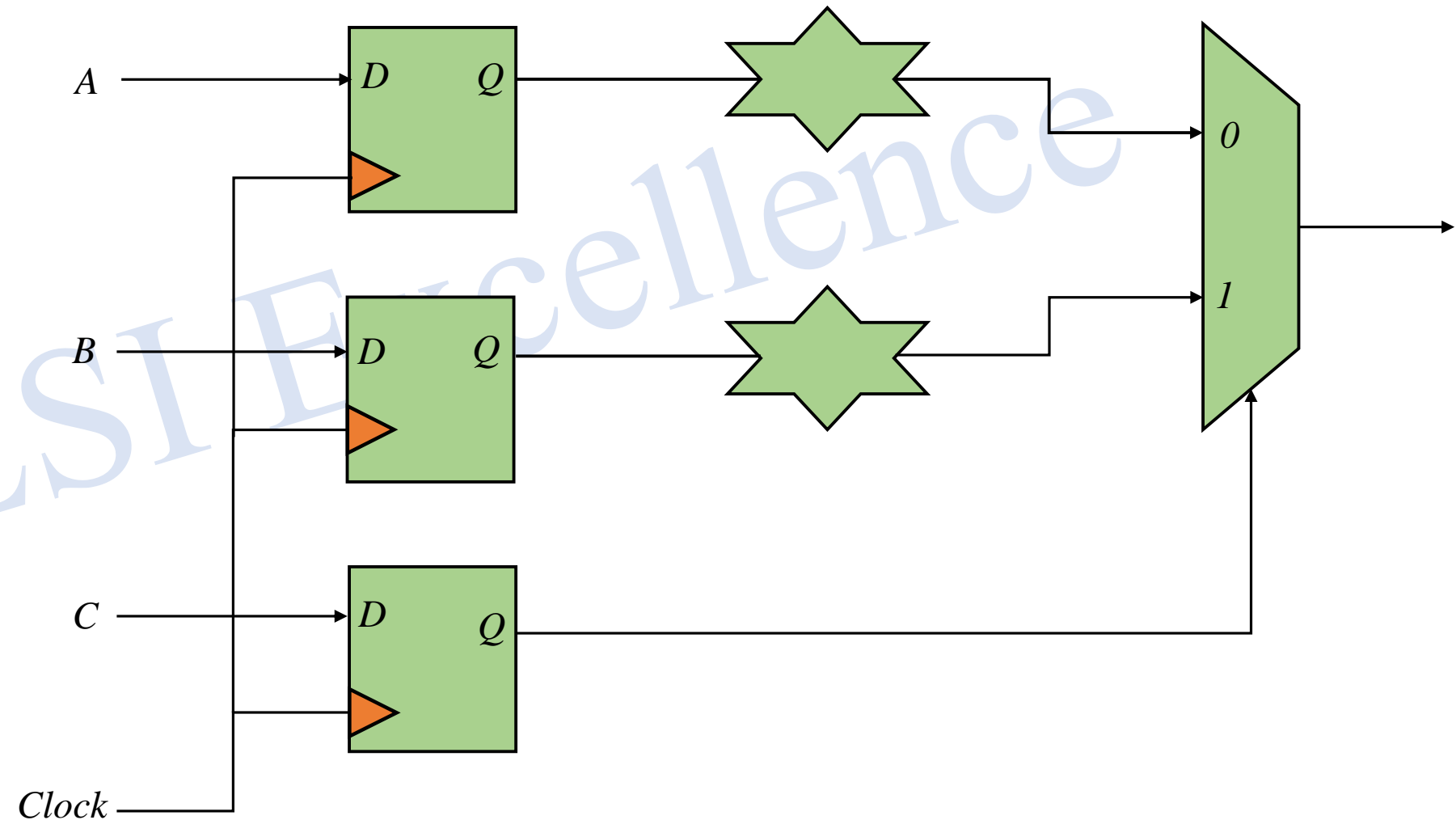


# VLSI Low Power Design : Interview Question #04


*Video Lecture [Link](#)*

# VLSI Low Power Design : Interview Question #04

Optimize the given circuit for minimum power consumption !


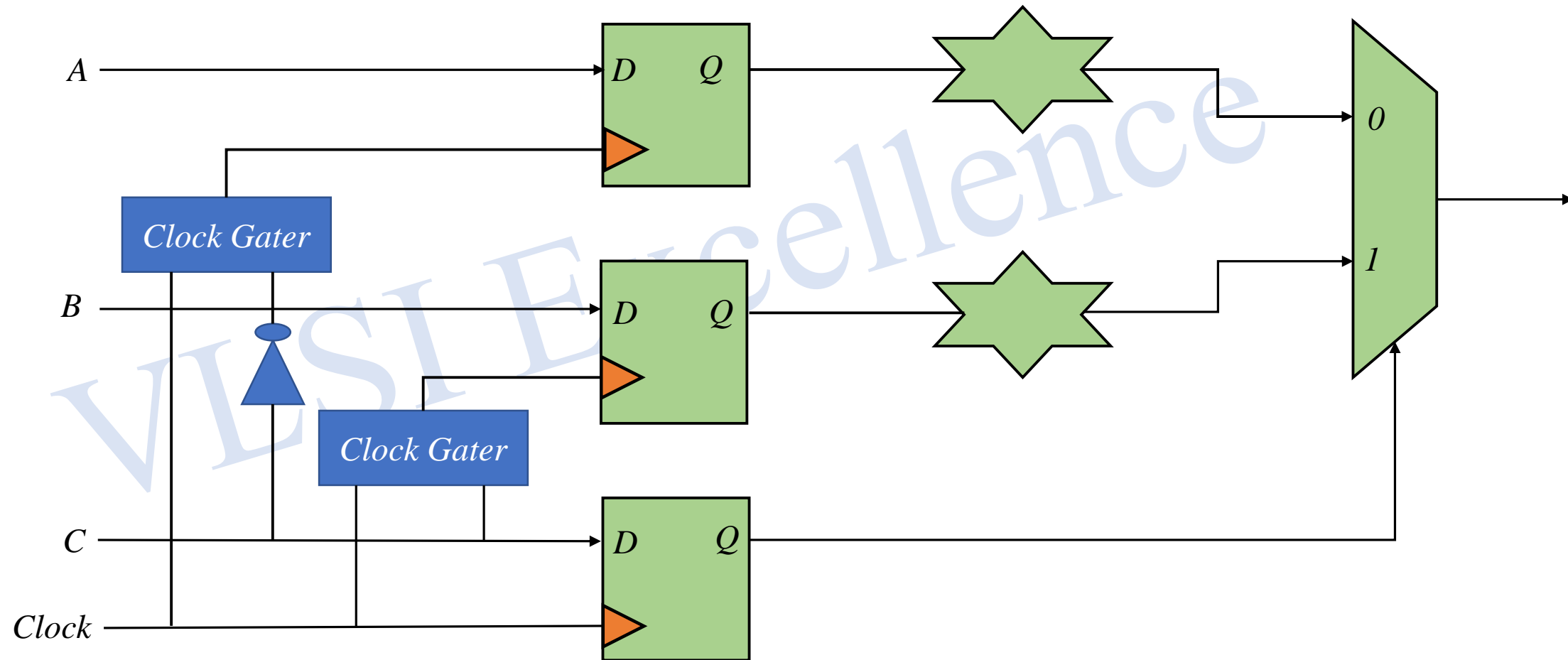
# VLSI Low Power Design : Interview Question #04 - **Solution**



## VLSI Low Power Design : Interview Question #04- Trade-Off

1. **Area Impact** – Two Additional Clock Gater and one NOT Gate added

VLSI Excellence

# Best Free VLSI Content

1. Verilog HDL Crash Course – [Link](#)
2. Static Timing Analysis (STA) – Theory Concepts – [Link](#)
3. Static Timing Analysis (STA) – Practice/Interview Questions – [Link](#)
4. Low Power VLSI Design – Theory Concepts – [Link](#)
5. Low Power VLSI Design (LPVLSI) – Practice/Interview Questions – [Link](#)
6. Digital ASIC Design Verilog Projects – [Link](#)

Please Like, Comment, Share & Subscribe [My Channel](#) in Order to Reach Out the Content to a Larger Audience.

Thanks !!